


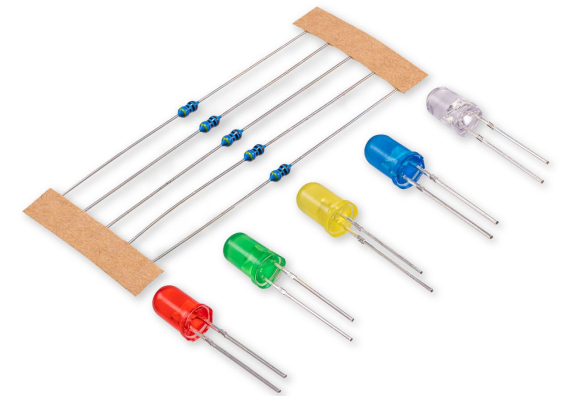
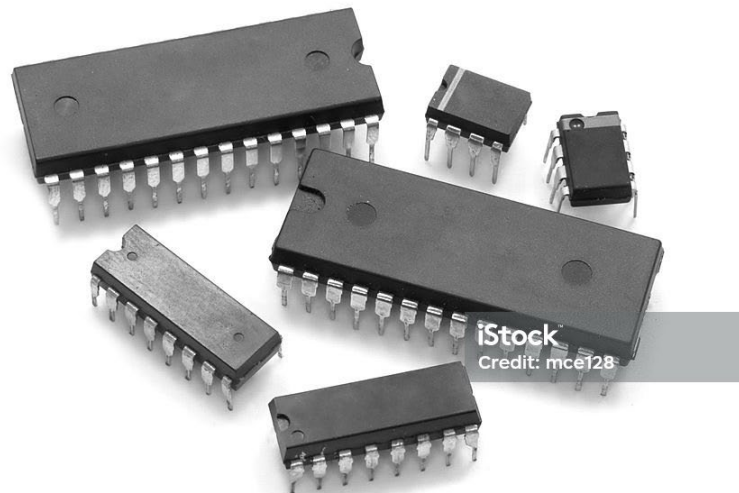
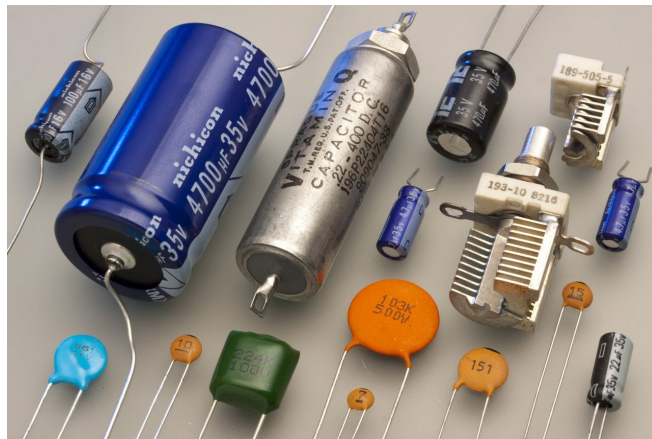
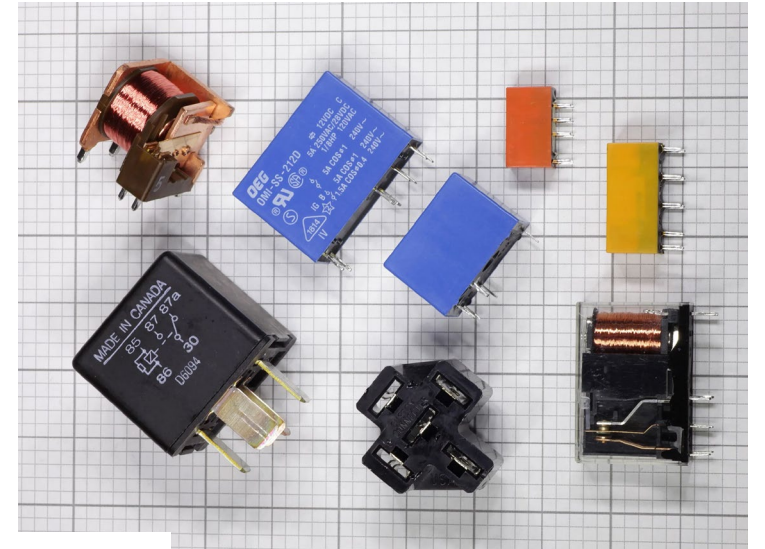
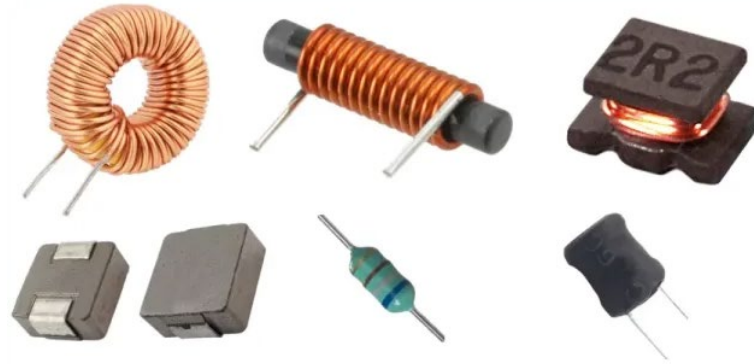


# Electronic components

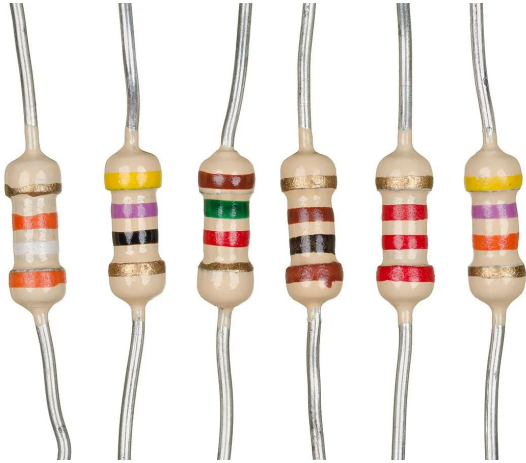

# Resistors

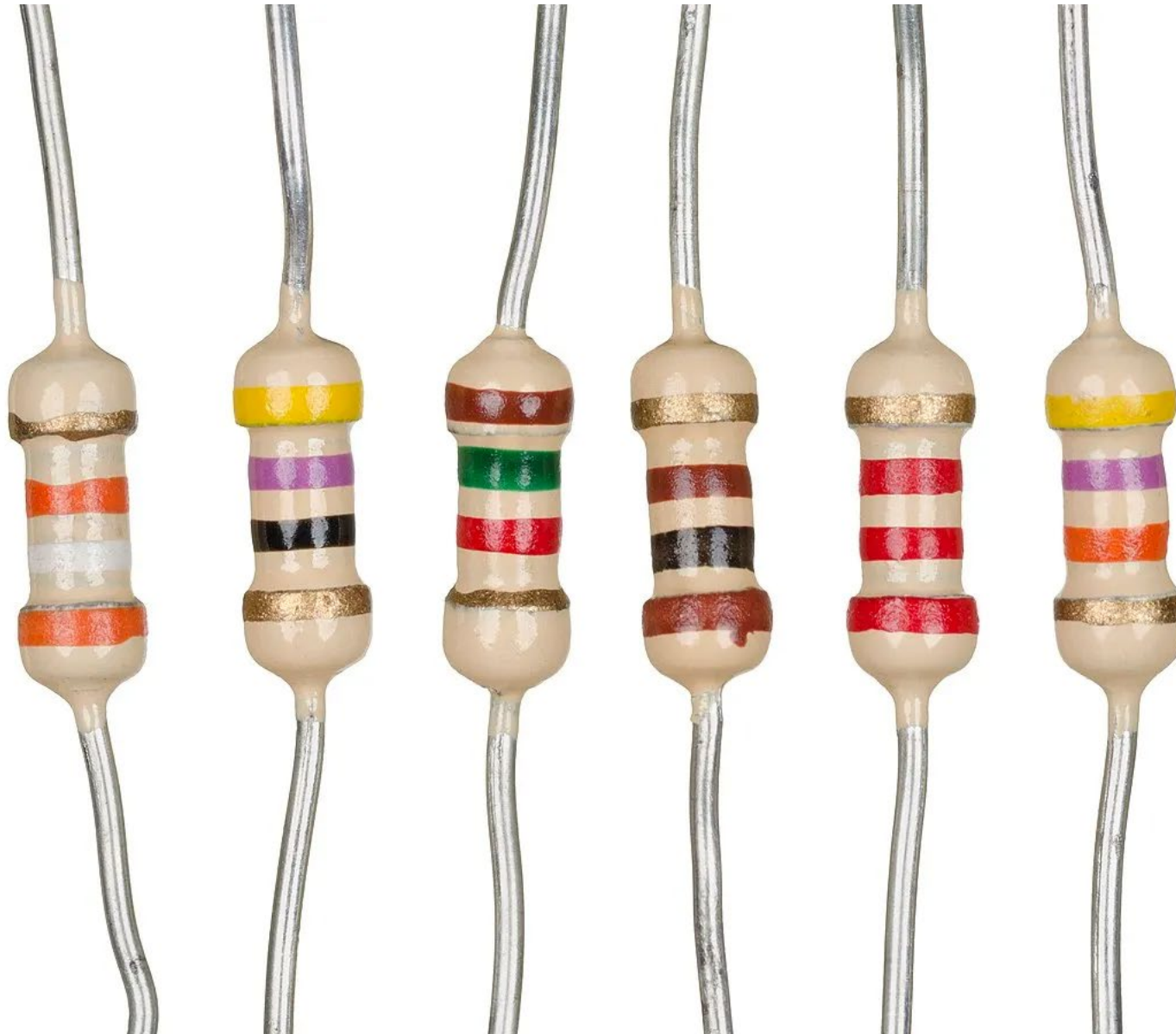

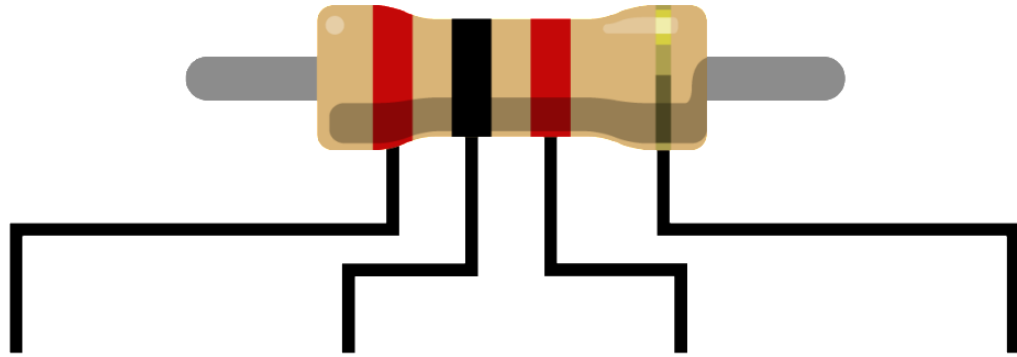


1st digit    2nd digit    Multiplier    Tolerance

0	0	x 1	±1%
1	1	x 10	
2	2	x 100	±2%
3	3	x 1K	
4	4	x 10K	
5	5	x 100K	
6	6	x 1M	
7	7		
8	8	x 0.1	±5%
9	9	x 0.01	±10%



# Wire wound resistors

$$R = \frac{\rho l}{A}$$

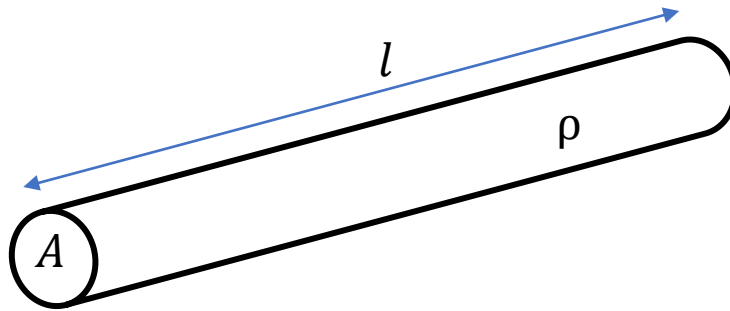

What is the resistance of 2 x 100m 2.5mm<sup>2</sup> cable.

$$R_{\text{cu}} = 1.724 \times 10^{-8}$$

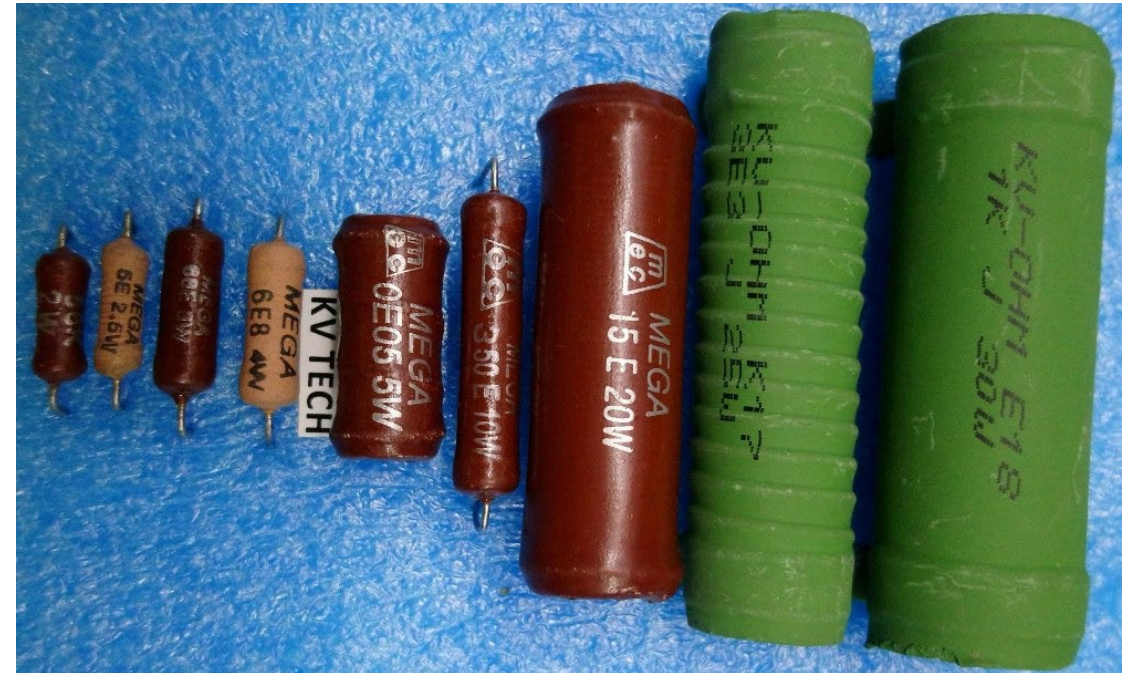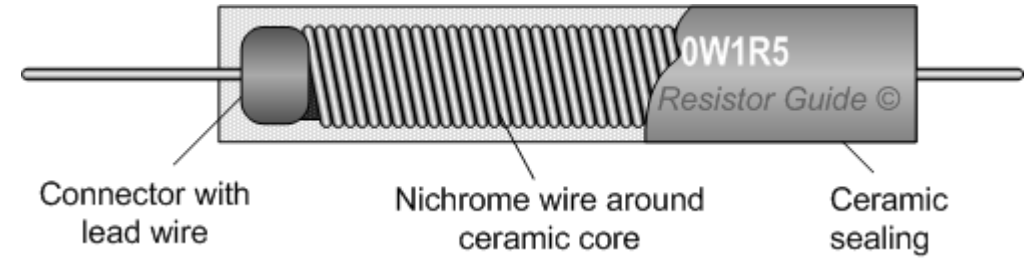





1/8 Watt Resistors



1/4 Watt Resistors



1/2 Watt Resistors







1 Watt Resistors




2 Watt Resistors



5 Watt Resistor

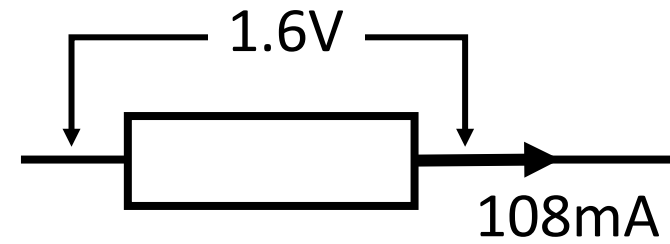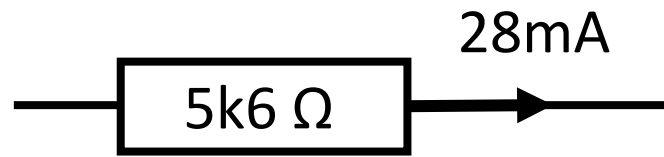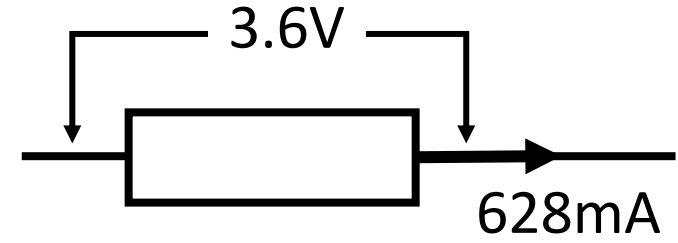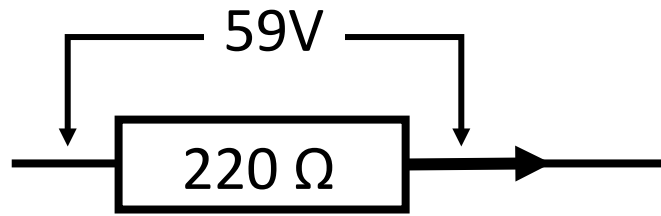

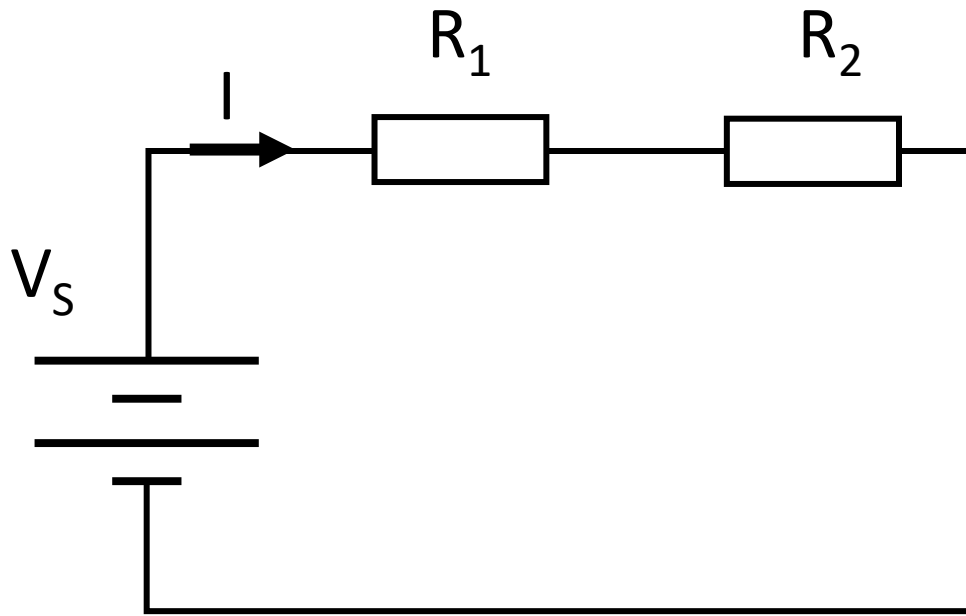

$$R_T = R_1 + R_2$$

$$I = \frac{V_S}{R_T}$$


$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$P_1 = IV_1$$

$$P_2 = IV_2$$

$$V_T = V_1 + V_2$$

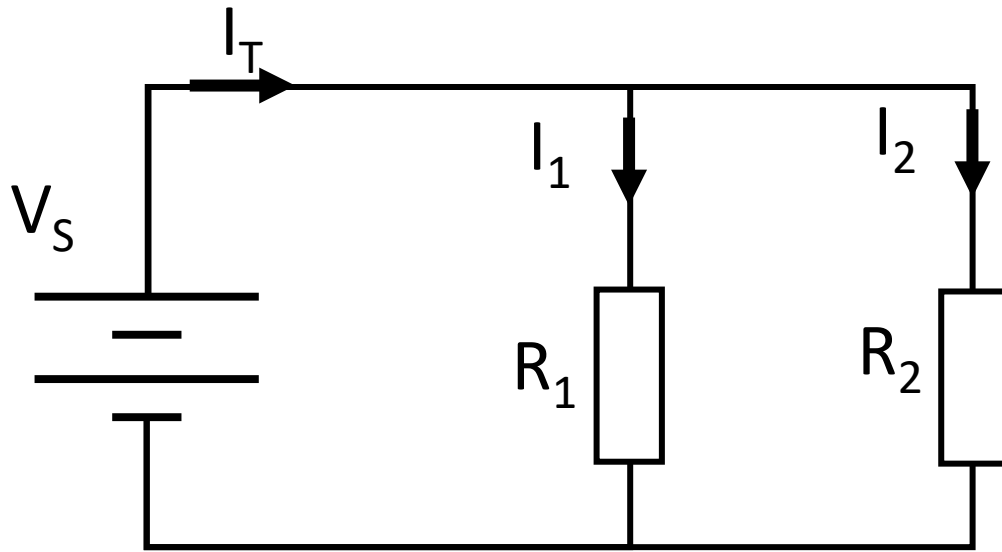

$$P_1 = I_1 V_S$$

$$P_2 = I_2 V_S$$


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I_T = \frac{V_S}{R_T}$$

$$I_1 = \frac{V_S}{R_1} \quad I_2 = \frac{V_S}{R_2}$$

$$I_T = I_1 + I_2$$



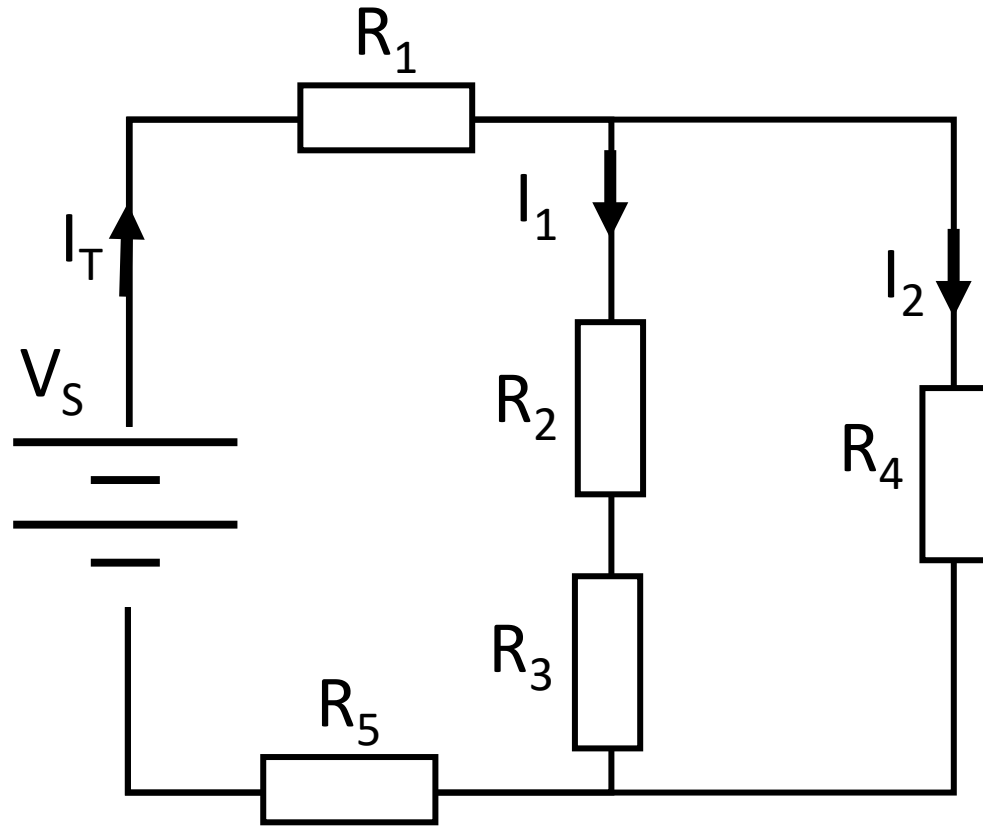


# Capacitors





Capacitor Type	Dielectric	Relative permittivity
Ceramic Class 1	Paraelectric (titanium dioxide)	12-90
Ceramic Class 2	Ferroelectric (barium titanate)	200-14,000
Film	Polypropylene (PP)	2.2
Film	Polyethylene terephthalate (PET)	3.3
Film	Polyphenylene sulfide (PPS)	3.0
Film	Polyethylene naphthalate (PEN)	3.0
Film	Polytetrafluoroethylene (PTFE)	2.0
Paper	Waxed paper	3.5-6.0
Aluminum electrolytic	Aluminum oxide	9.6
Tantalum electrolytic	Tantalum pentoxide	26
Niobium electrolytic	Niobium pentoxide	42
Glass	Glass	3.7-10
Mica	Mica	5-8

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$\epsilon_0 = 8.85 \times 10^{-12}$$

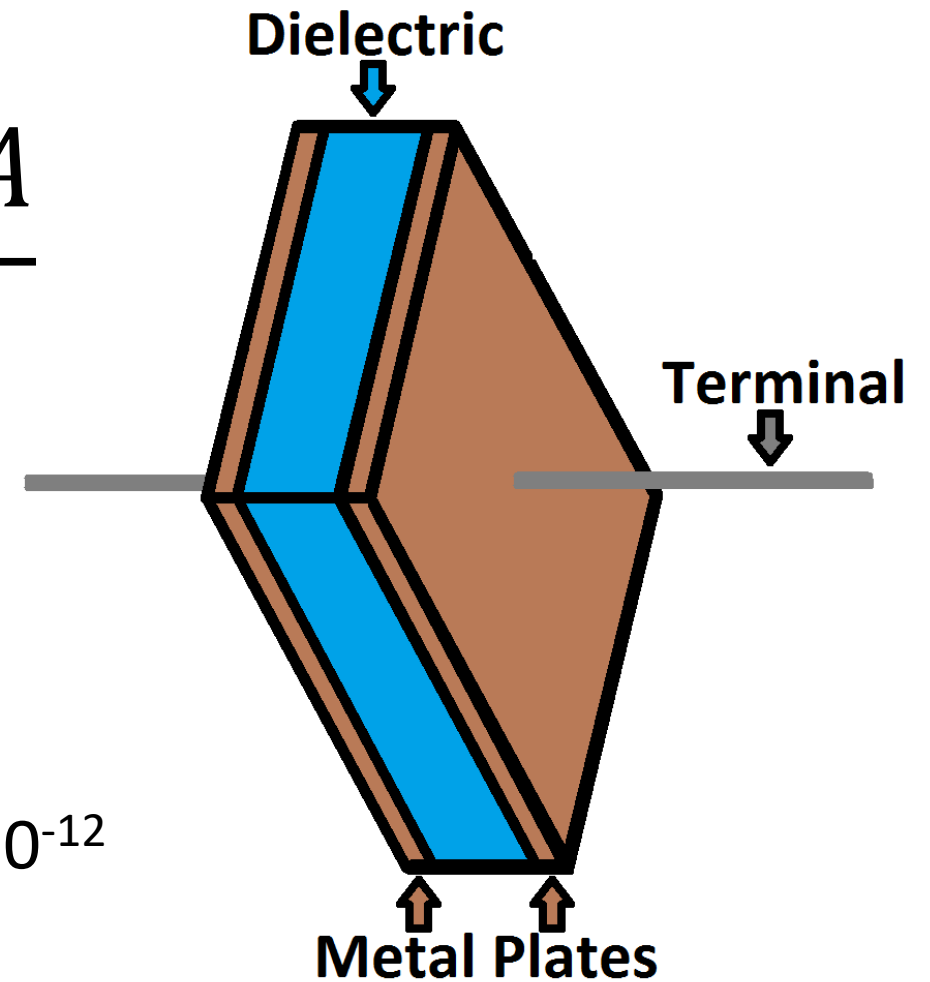

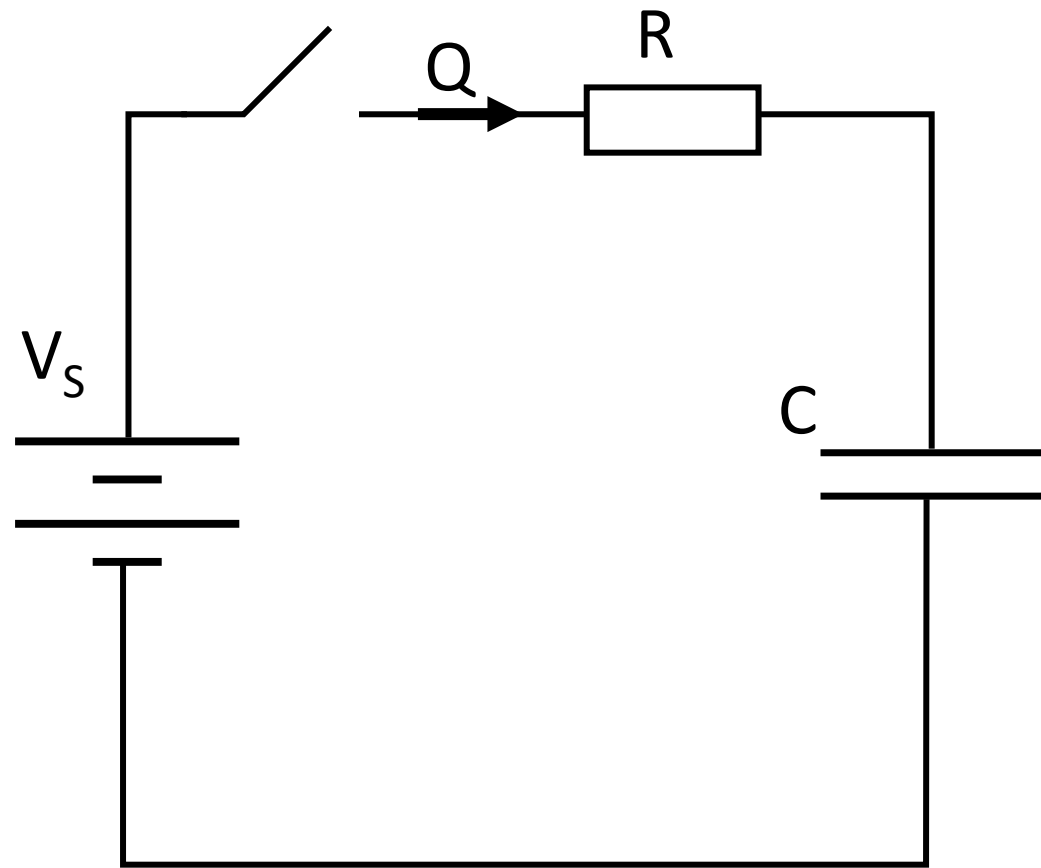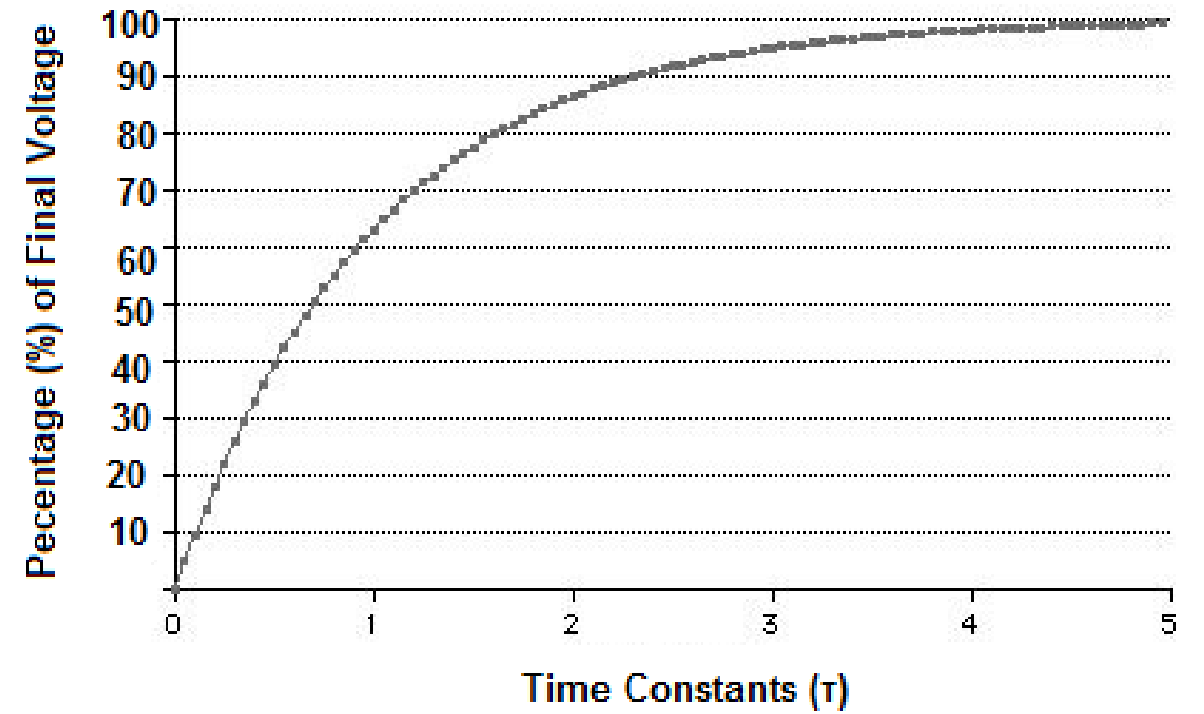**Capacitor Charging Graph**

$$E = \frac{CV^2}{2}$$

So how much energy could this capacitor have?




# Inductors

$$L = \frac{N^2 \mu_0 \mu_r A}{l}$$

$$\mu_0 = 4\pi \times 10^{-7}$$


Material	$\mu_r$
Vacuum	1
Air	1.00000037
Copper	0.999994
Aluminum	1.000022
Carbon steel	100
Iron (99.8% pure)	5000
Permalloy	100000

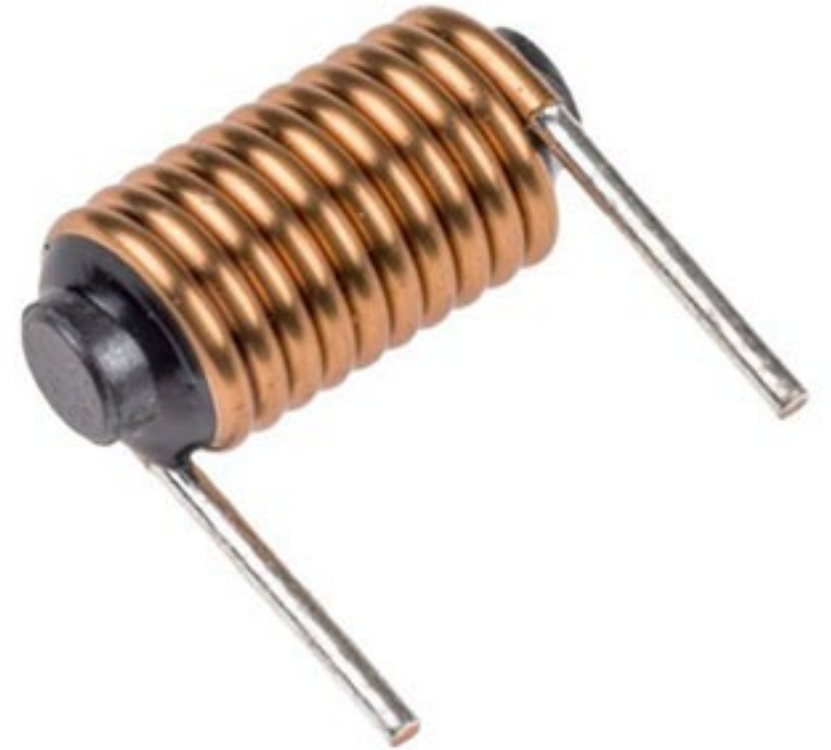




# Inductors

$$E = \frac{LI^2}{2}$$

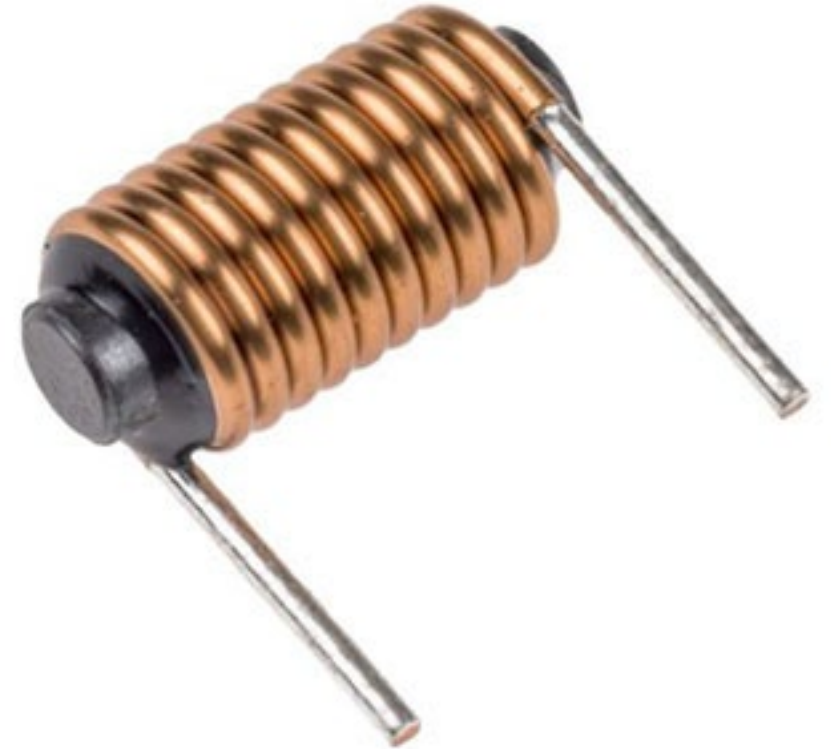


OFFICIAL

# IC's and Logic gates

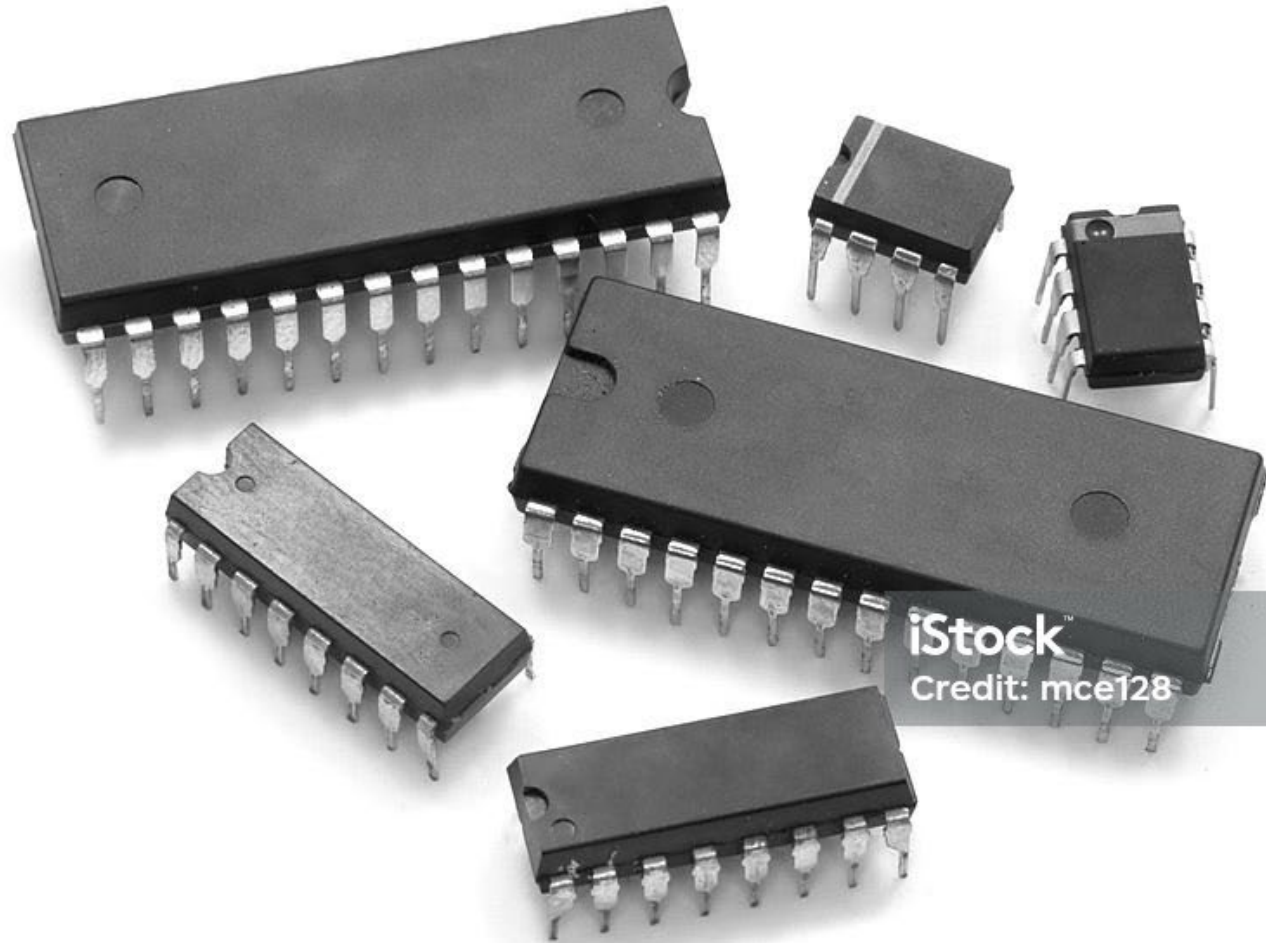


iStock  
Credit: mce128

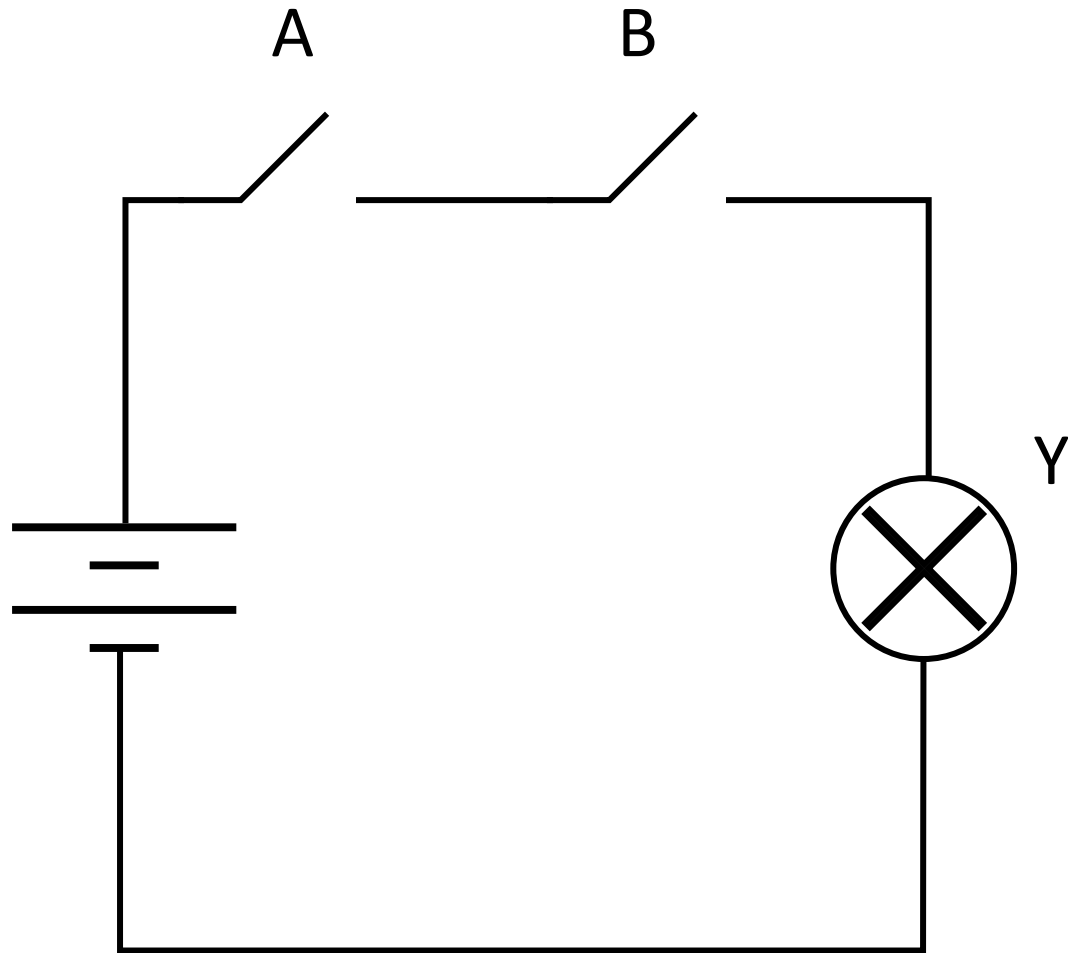

Logic  
**AND**


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

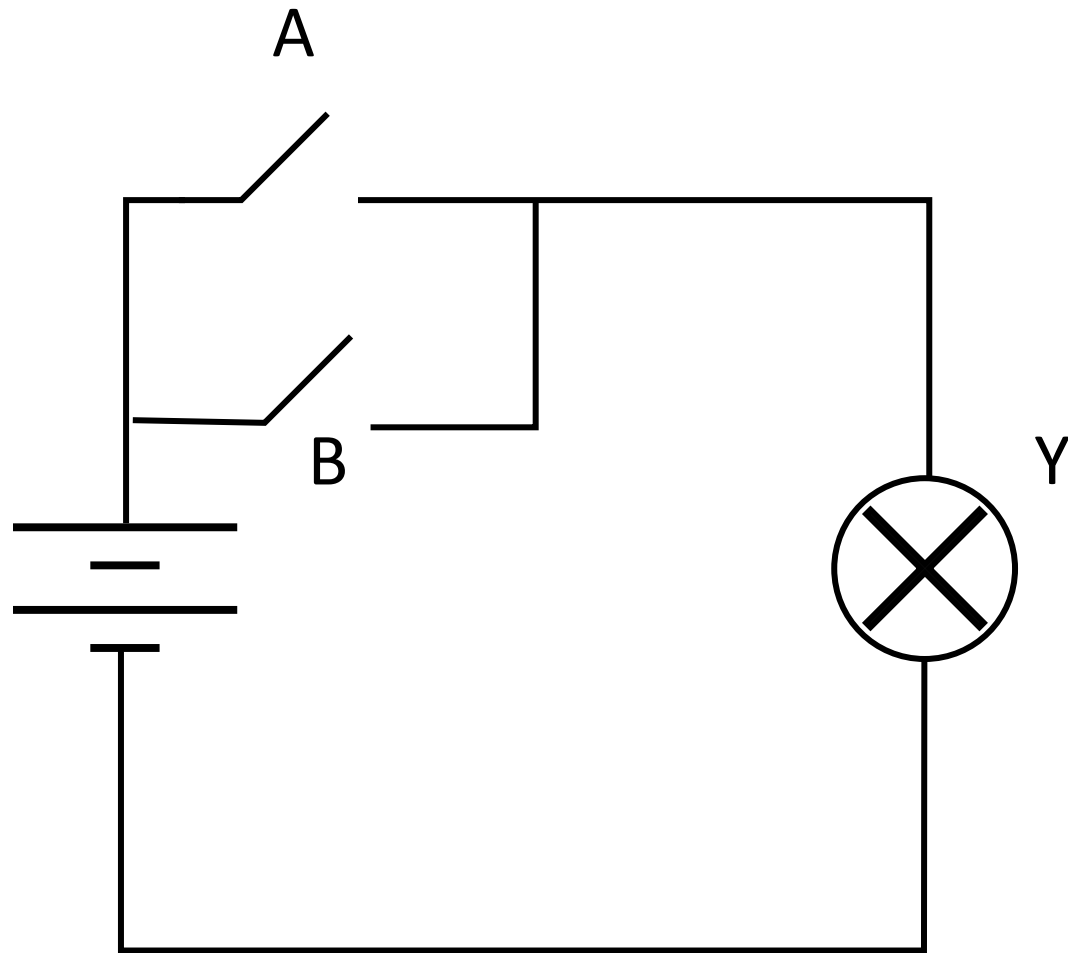

Logic

**OR**


<b>A</b>	<b>B</b>	<b>Y</b>
0	0	0
0	1	1
1	0	1
1	1	1

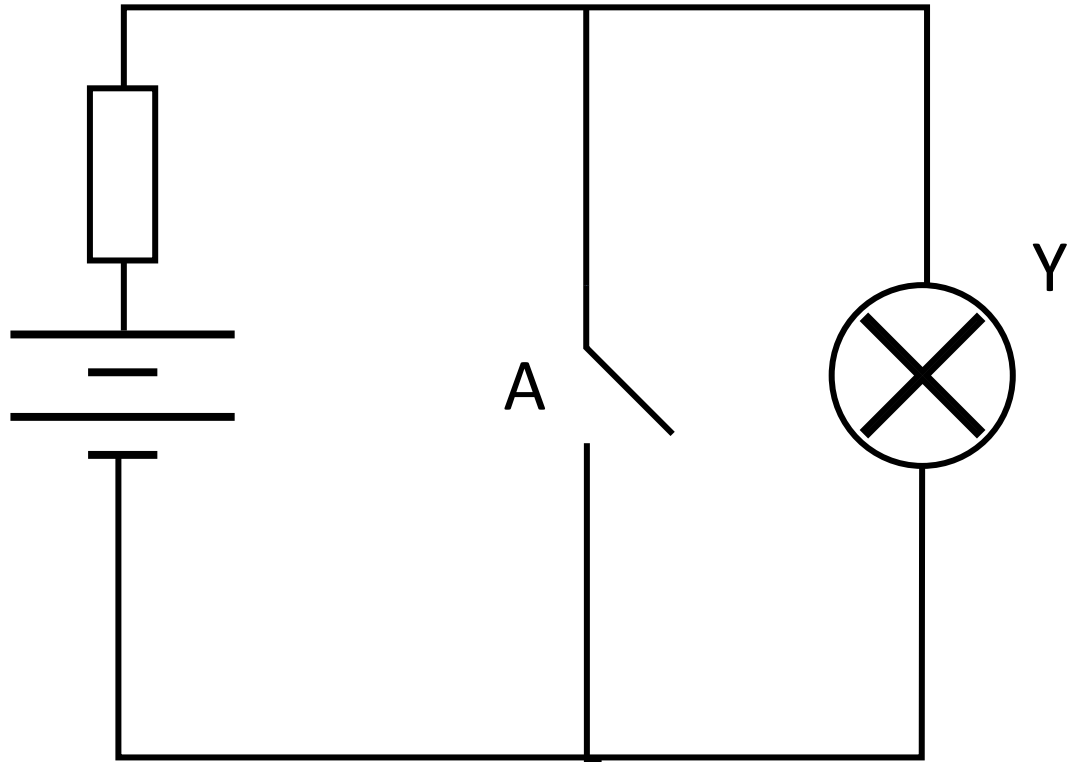

Logic  
**NOT**

<b>A</b>	<b>Y</b>
0	1
1	0


Logic  
**NAND**

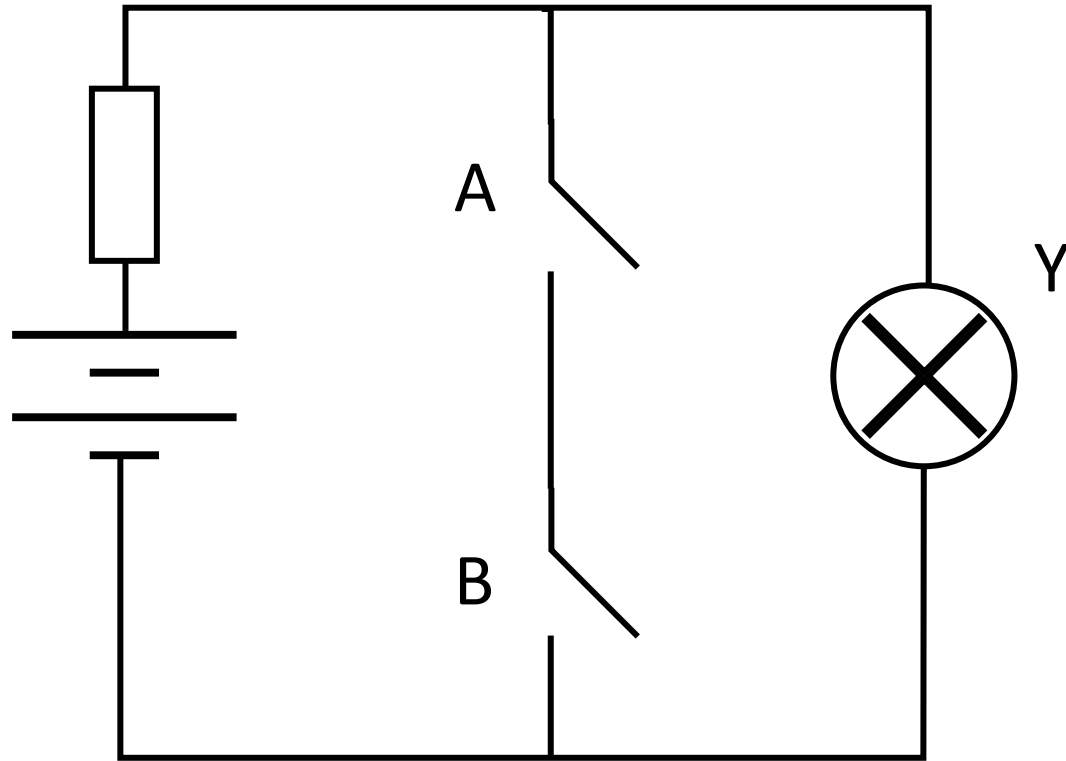



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



AND

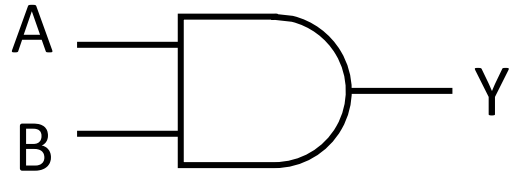


NOT

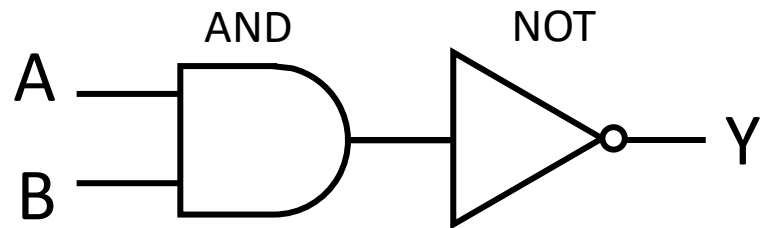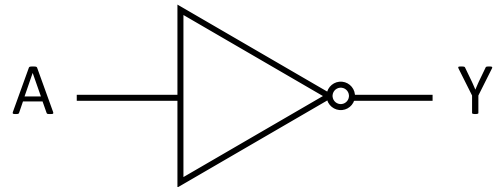Logic  
NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND

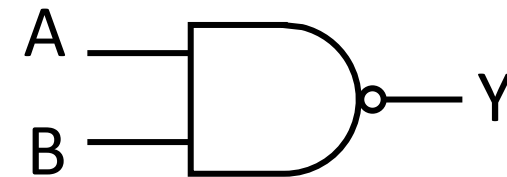


# Faults in electronic equipment

Failures can be caused by;

- excess temperature,
- excess current or voltage,
- ionizing radiation,
- mechanical shock, stress or impact, and many other causes.

In semiconductor devices, problems in the device package may cause failures due to;

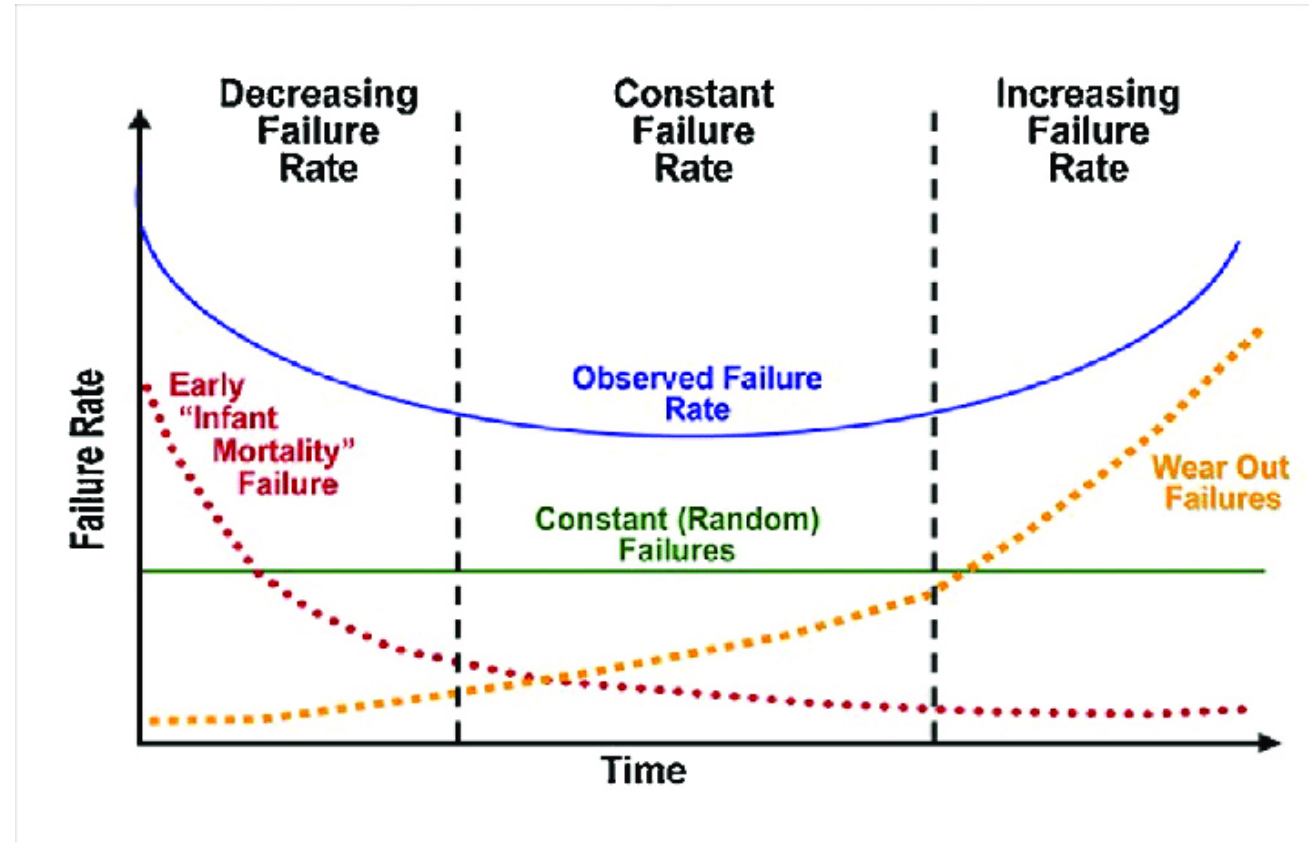- contamination,
- mechanical stress of the device, or
- open or short circuits or
- electrostatic discharge (ESD)



# Capacitor Failure


Failures caused by capacitor damage are the highest among electronic devices, and damage to electrolytic capacitors is the most common.

Capacitor damage is manifested as: the capacity becomes smaller, the capacity is completely lost, the leakage, and the short circuit.

The life of a capacitor is directly related to the ambient temperature. **The higher the ambient temperature, the shorter the life of the capacitor.** This rule applies not only to electrolytic capacitors, but also to other capacitors.

Therefore, when looking for a faulty capacitor, you should focus on **checking the capacitors that are close to the heat source**, such as the capacitors next to the heat sink and high-power components.

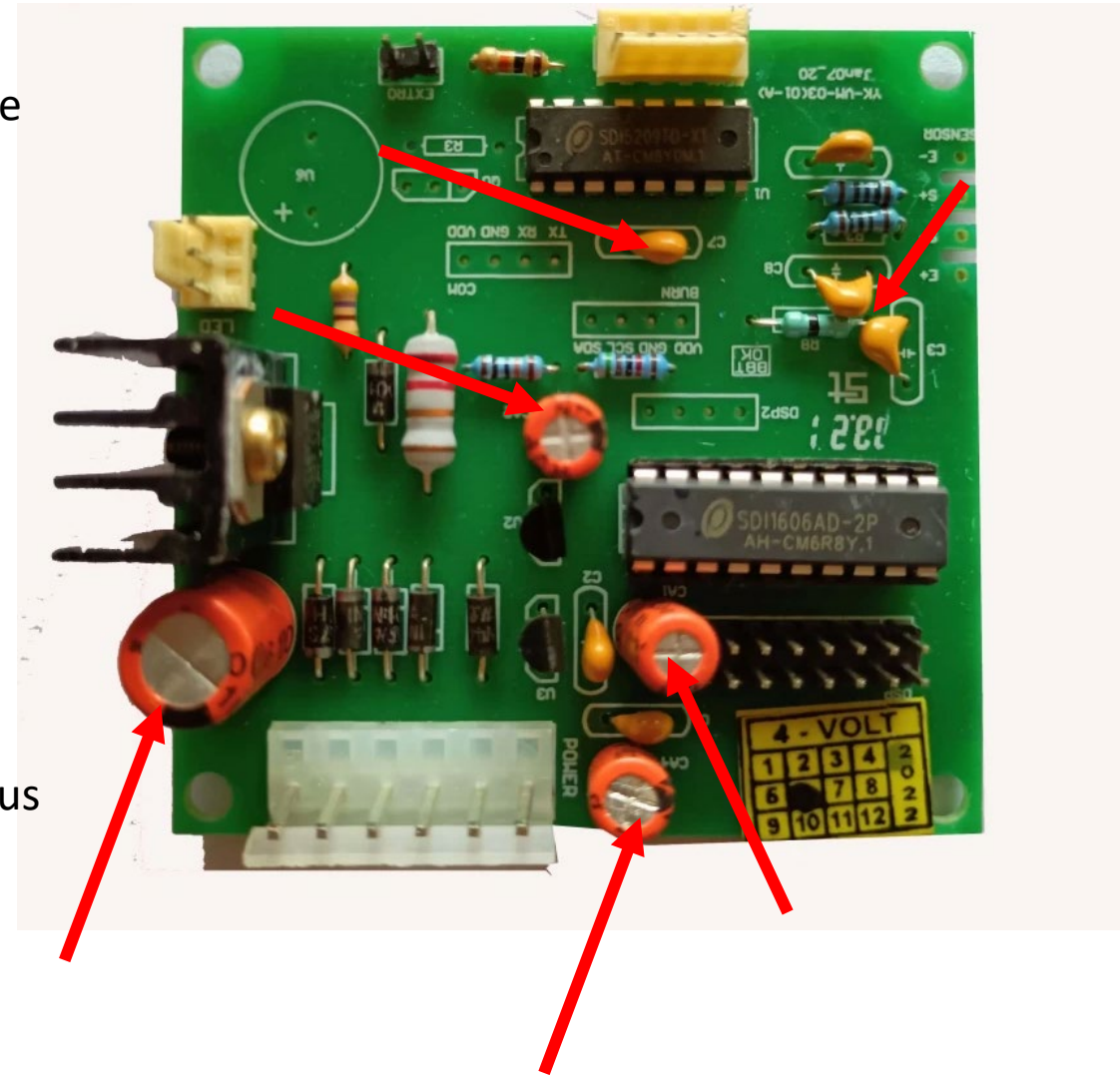Using electronics in a cool, dry environment can prevent damage from excessive heat and humidity.




## Resistor Failure

Resistance is the most numerous component in electrical equipment, but it is not the component with the highest damage rate.


Open circuit is the most common type of resistance damage. It is rare that the resistance value becomes larger, and the resistance value becomes smaller.

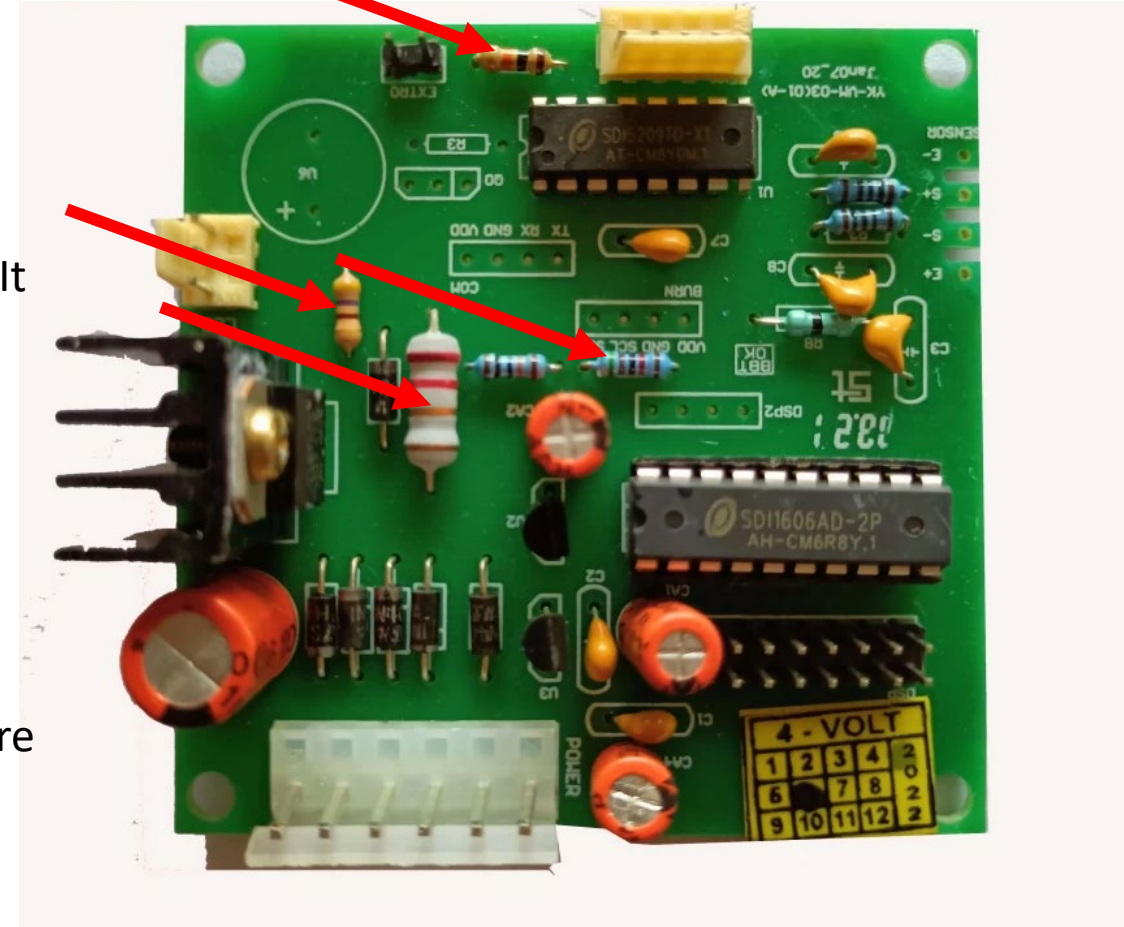According to the characteristics listed above, we can first observe whether the low-resistance resistors on the circuit board have burnt black marks, and then according to the characteristics that most of the resistors are open or the resistance becomes larger, and the high-resistance resistors are easily damaged.


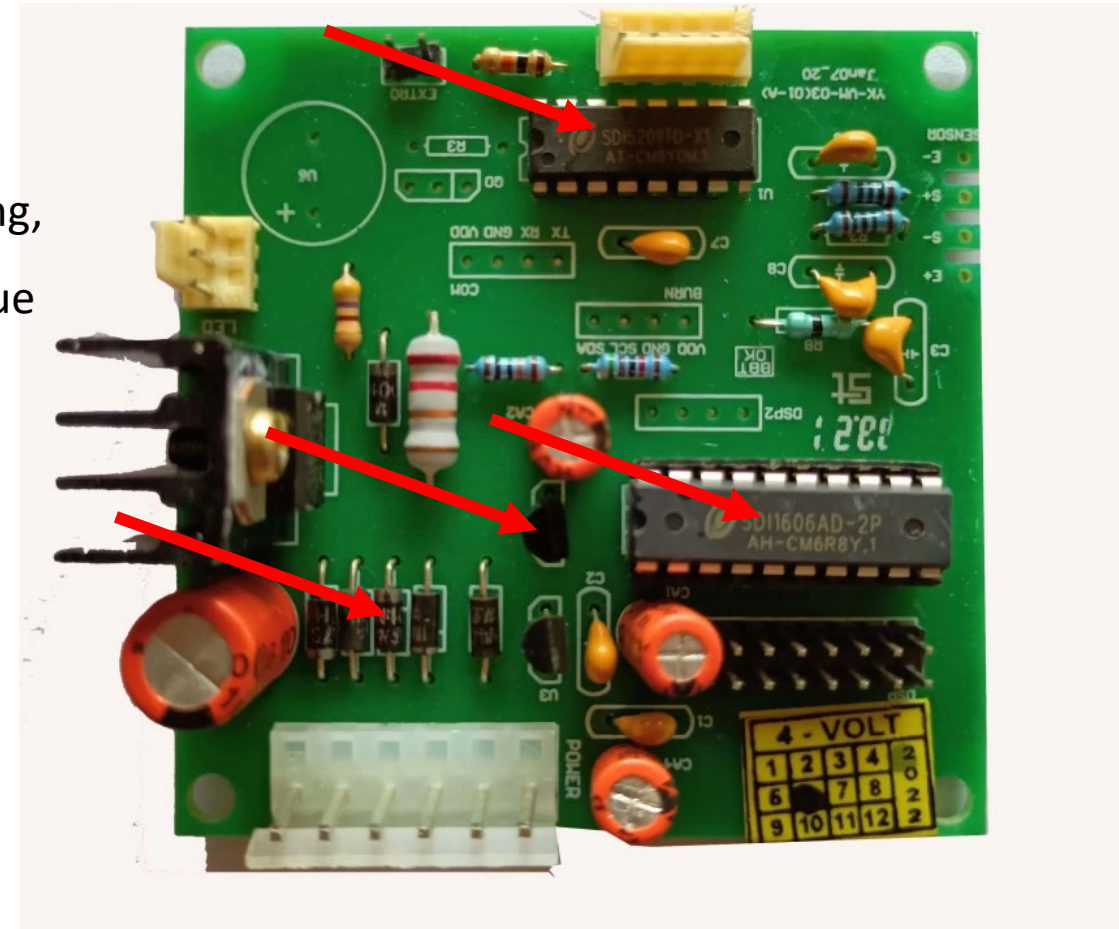
# Semiconductor Failure

- Cracking of encapsulation due to thermal overstress
- Penetration of moisture, flux contaminants during soldering, washing of boards, storage under humid conditions, etc. due to seal integrity problems.
- Mechanical stress cracks due to differential thermal expansion of plastic encapsulant, metal leads, die.
- Design and fabrication faults, misalignment of layers, geometric Changes in threshold voltage/current characteristics with change of temperature.










## Other component failures

Terminals that get pressure as connectors are forced onto them

Heatsinks not properly bolted to the semiconductor and so does not allow heat to dissipate.

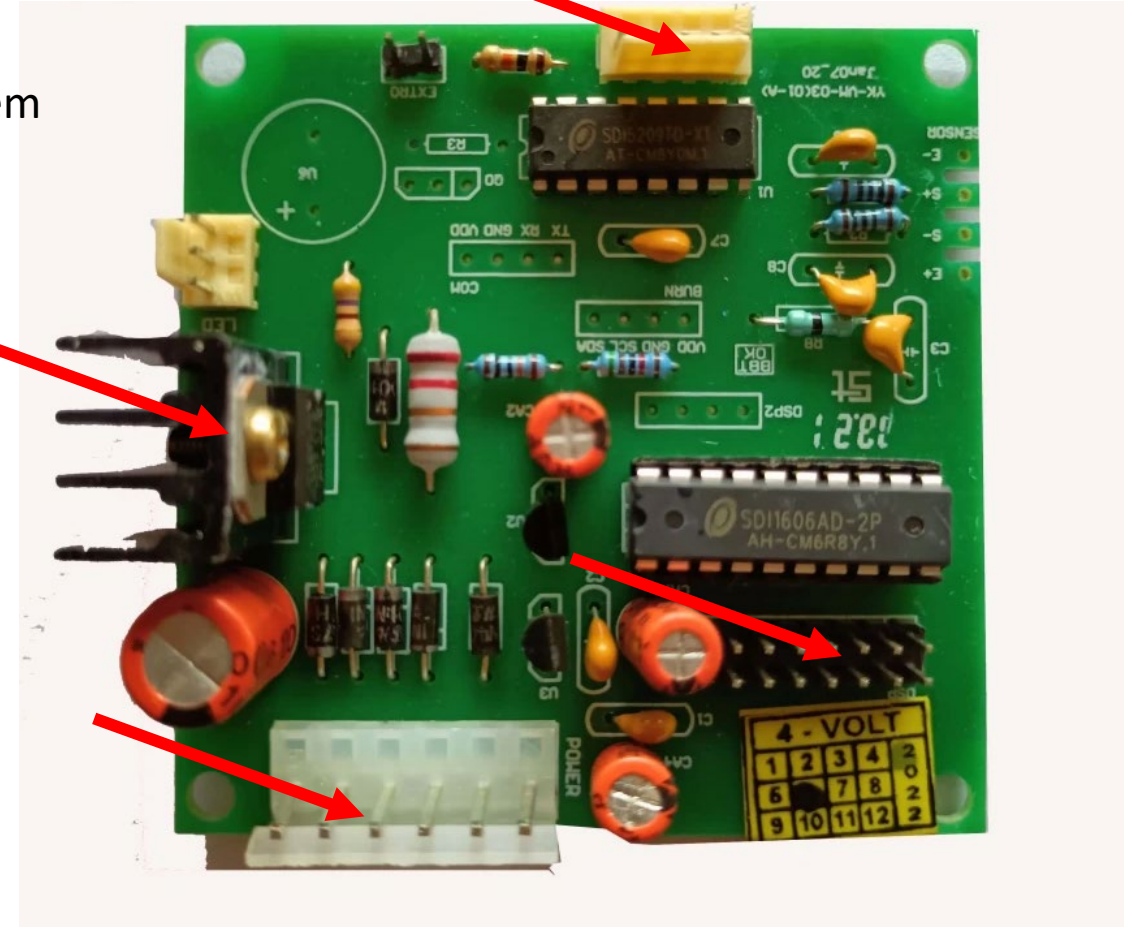Relays that are constantly used and have carbonized contacts



# Analyse Faults

There are techniques used to detect and analyze faults.

## **Visual inspection**

The first step in fault detection is to visually inspect the circuit for any obvious signs of damage, wear, or improper connections. You should look for things like broken wires, loose or corroded terminals, burned or cracked components, solder bridges, or foreign objects. You should also check the polarity and orientation of components, such as diodes, transistors, or ICs.

## **Multimeter testing**

The next step in fault detection is to use a multimeter to measure the voltage, current, or resistance of the circuit or its components. A multimeter is a handy tool that can help you verify the power supply, check the continuity of wires and traces, or find short circuits or open circuits.

## **Oscilloscope analysis**

The third step in fault detection is to use an oscilloscope to observe the waveform of the signals in the circuit. An oscilloscope is a device that can display the voltage and time of a signal on a screen, allowing you to see its shape, frequency, amplitude, phase, or distortion. You can use an oscilloscope to compare the input and output signals of a circuit or a component, or to find noise, glitches, or anomalies in the signals.


## Logical troubleshooting

The final step in fault detection is to use logical troubleshooting to isolate and identify the cause of the fault.



Logical troubleshooting is a process of applying your knowledge of the circuit's function, design, and behavior to narrow down the possible sources of the fault.

You can use a divide-and-conquer approach, where you split the circuit into smaller sections and test each one separately, or a hypothesis-and-test approach, where you formulate a possible explanation for the fault and verify it with experiments.

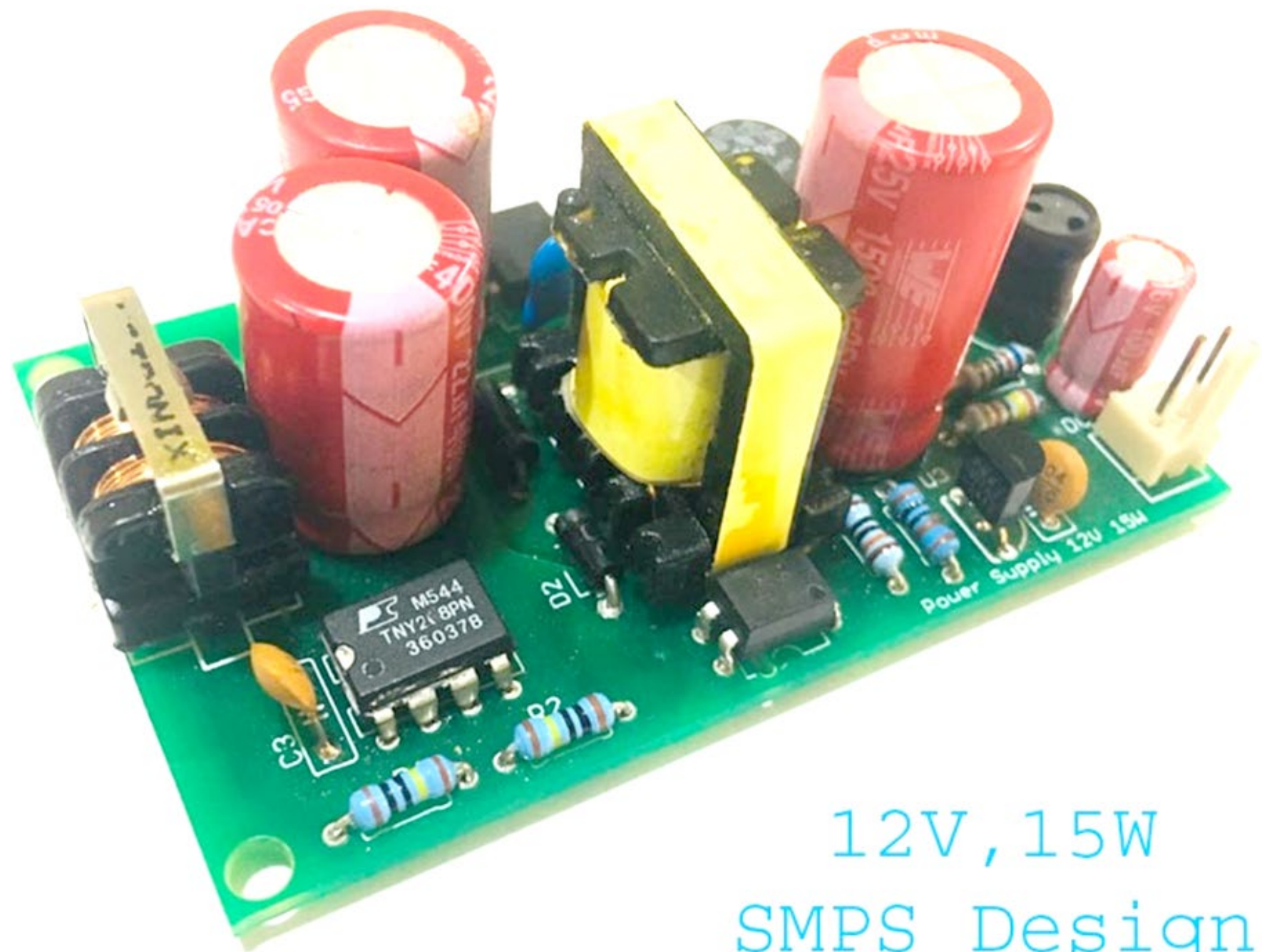You can also use schematics, datasheets, or manuals to help you understand the circuit and its components.



12V, 15W  
SMPS Design

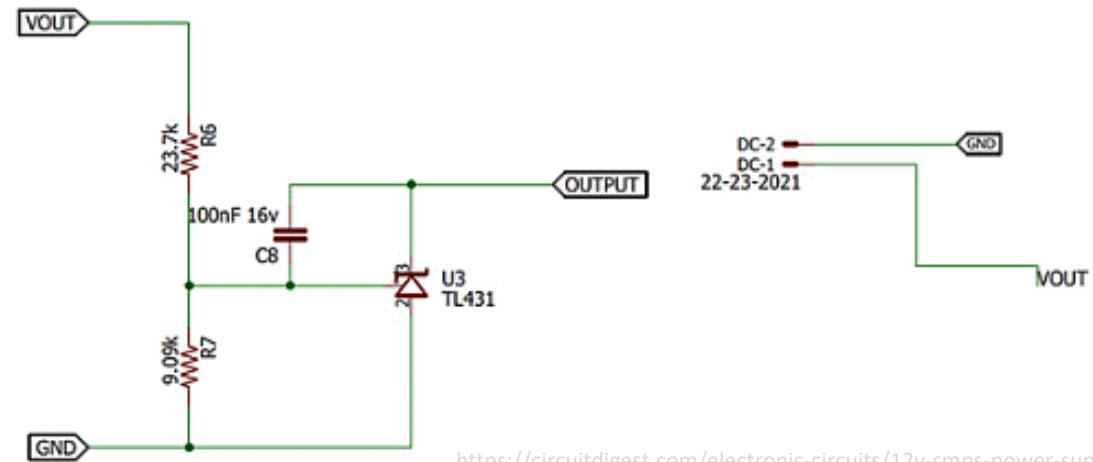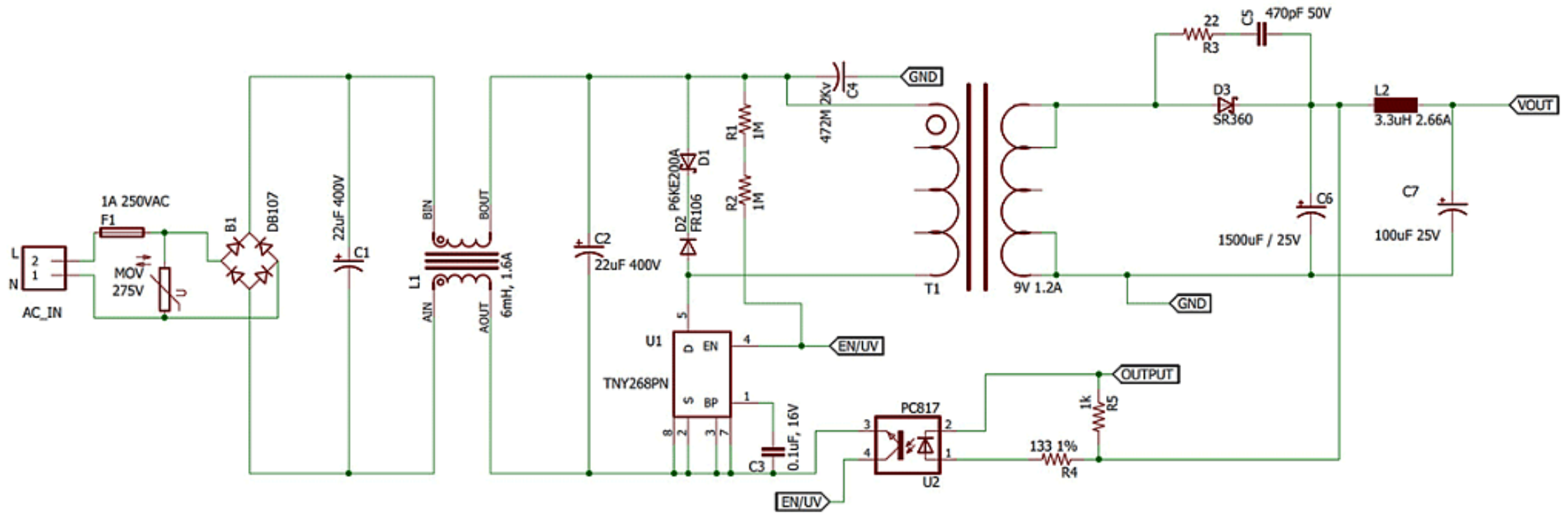




# ALARM SYSTEM COMPONENTS

## -Sensors
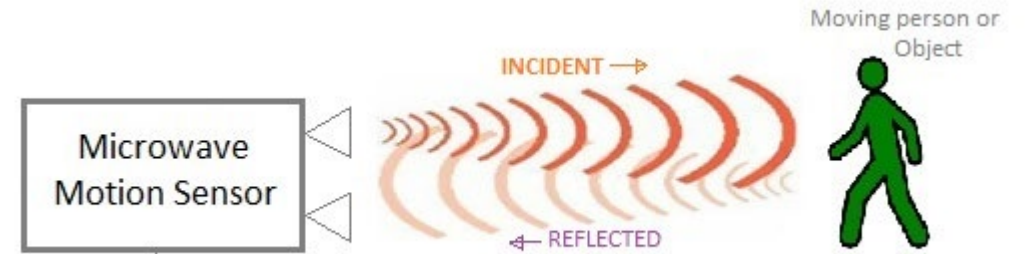
### MICROWAVE

These motion detectors emit microwave signals and measure the time taken for the signal to be reflected back to the sensor, this is known as the echo time. The echo time is used to calculate the distances from all the stationary objects in the detection zone, to establish a baseline to work from.

A person moving into the detection zone causes a disruption in the microwave beam, changing the echo time and triggering the lights.




### PIR

These sensors detect heat. They do this by measuring the ambient temperature of the room using several detection beams.

When a difference in temperature is detected by one of the beams, the sensor is activated, switching on the lights.

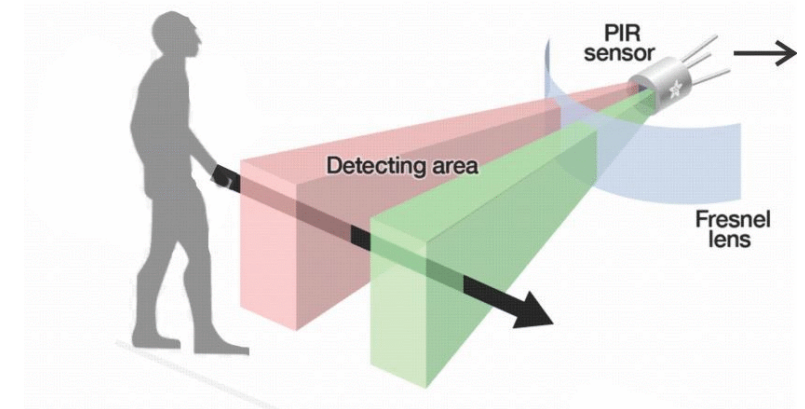When all the beams sense the same temperature again, the lights will switch off.






# ALARM SYSTEM COMPONENTS


## -PIR Sensors
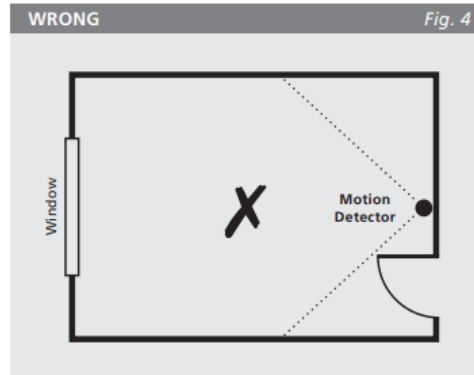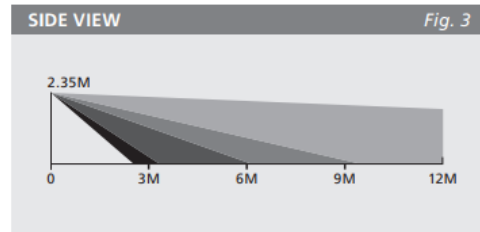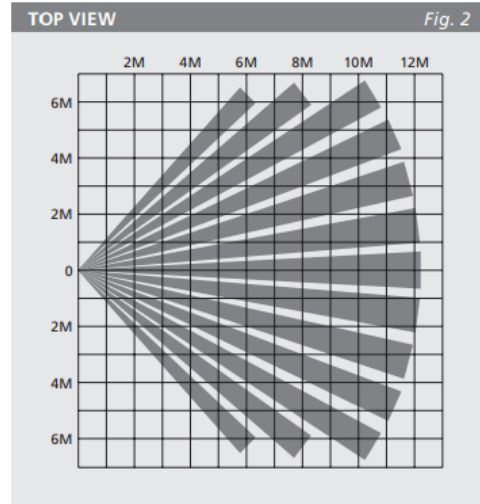
### LOCATING THE MOTION DETECTORS


Your detectors have been preset to Normal Setting (fast) – covering a plan area of approximately 12 metres x 12 metres. If you have pets in the house while the alarm is on, refer to page 24 to set the detectors to a Pet Friendly Setting (slow). Pet coverage is approximately 10.5 metres x 10.5 metres.



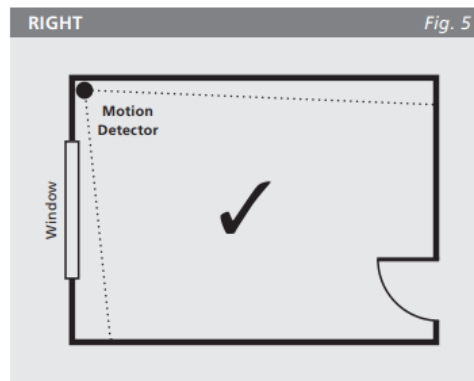Do not locate detectors opposite windows and in middle of rooms. Reflective surfaces can cause false alarms.



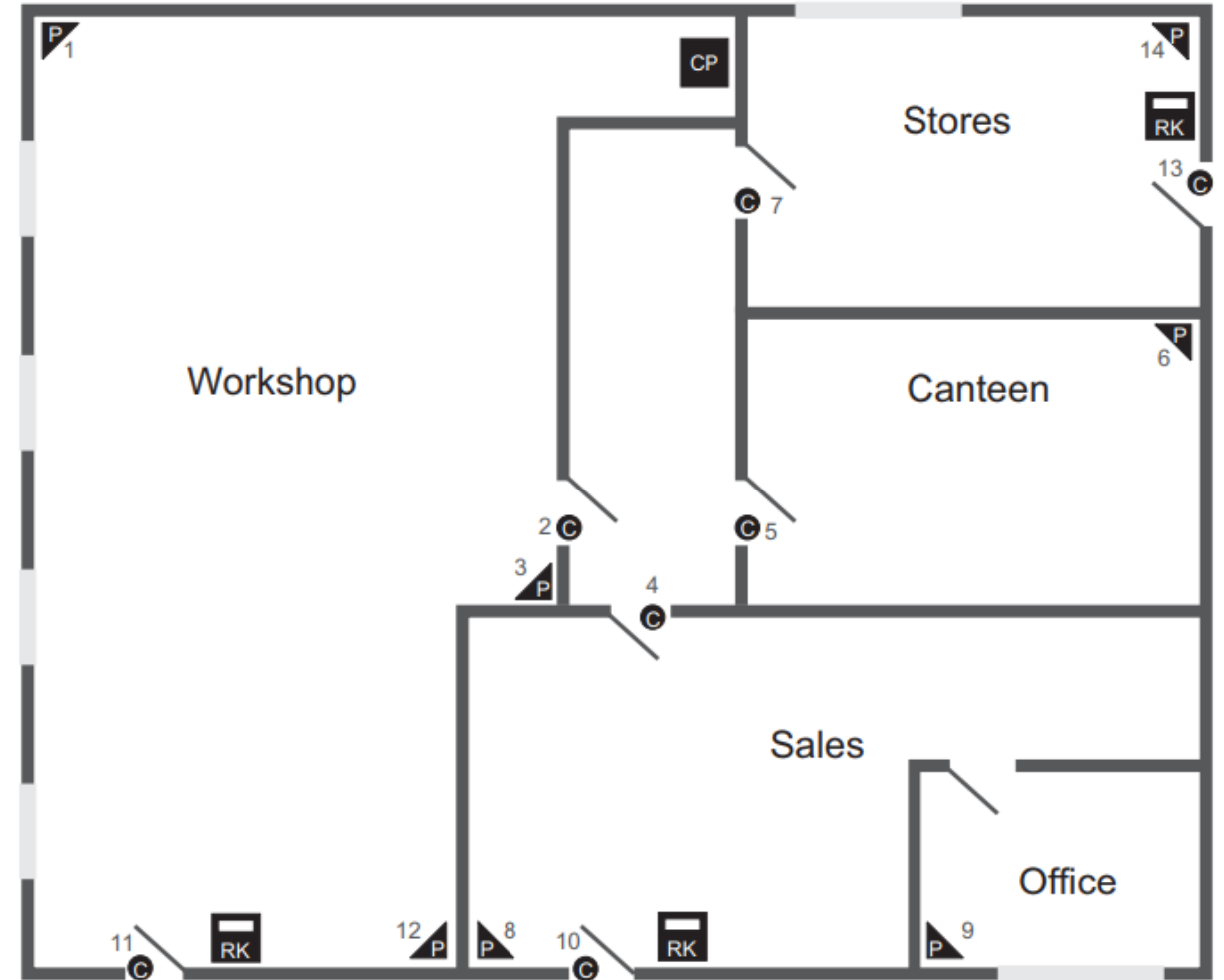Locate detectors diagonally opposite doors and in corner of room.




KEY:

- Passive Infra-Red detector
- Magnetic Contact
- Remote Keypad
- Control Panel




# PIR Sensors

OFFICIAL

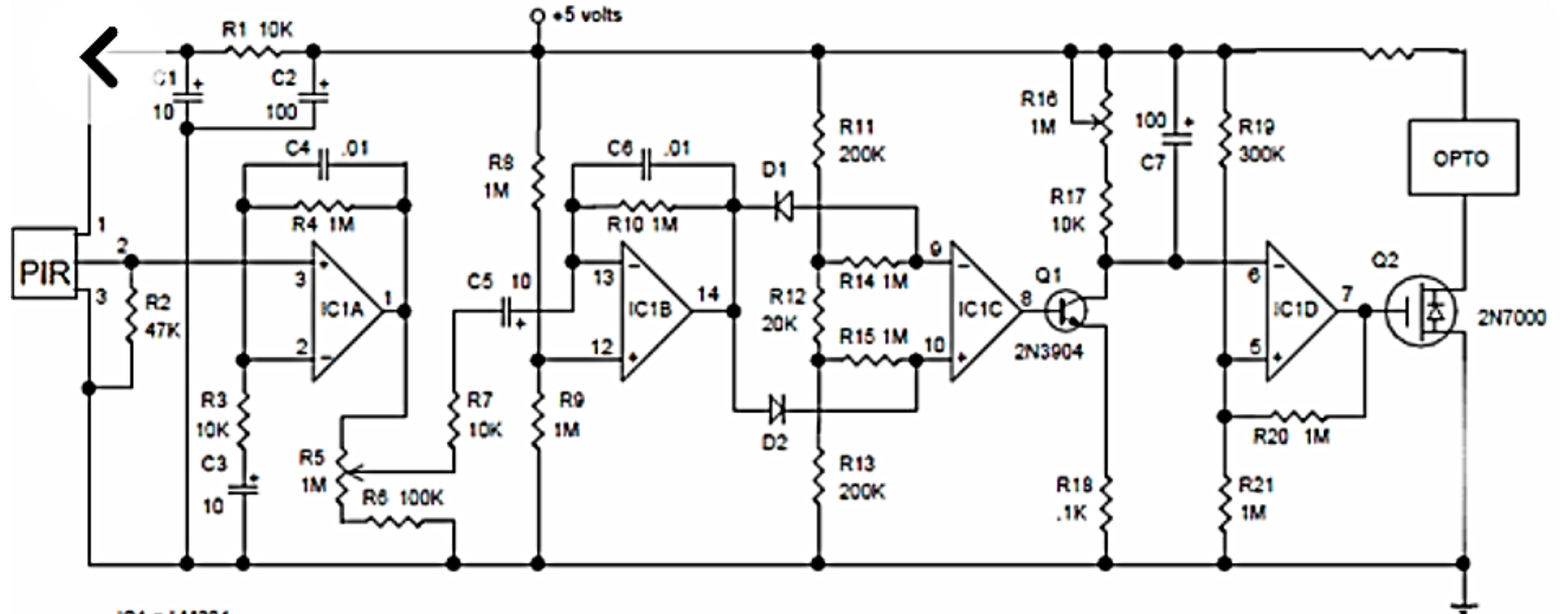

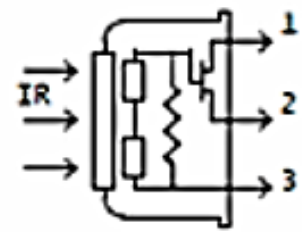- IC1 = LM324
- D1, D2 = 1N914
- RY1 = 5 VOLT SPDT RELAY
- PIR = RE200B PYROELECTRIC SENSOR



OFFICIAL